

### Effect of Dielectrics

- Electric Dipole Moment – permanent separation of charge in polar or dipole molecules. (e.g. water)
- Other dielectrics are non-polar, they can achieve temporary polar characteristics by induction

TABLE 17-2  
Dipole Moments  
of Selected Molecules

Molecule	Dipole Moment (C·m)
$\text{H}_2^{(+)}\text{O}^{(-)}$	$6.1 \times 10^{-30}$
$\text{H}^{(+)}\text{Cl}^{(-)}$	$3.4 \times 10^{-30}$
$\text{N}^{(-)}\text{H}_3^{(+)}$	$5.0 \times 10^{-30}$
$>\text{N}^{(-)}-\text{H}^{(+)}$	$\approx 3.0 \times 10^{-30}$
$>\text{C}^{(+)}=\text{O}^{(-)}$	$\approx 8.0 \times 10^{-30}$

<sup>†</sup>These groups often appear on larger molecules; hence the value for the dipole moment will vary somewhat, depending on the rest of the molecule.

### Effects of Dielectrics

- Slab polarized by induction
- Surfaces become charged
  - result from dipole moments of dielectric molecules
  - NOT* from transfer of electrons

### Effects of Dielectrics


- Elec. field in slab by surface charge opposes the external field
- $E =$  vector sum

### Effects of Dielectrics


- Elec. field in slab by surface charge opposes the external field
- $E =$  vector sum
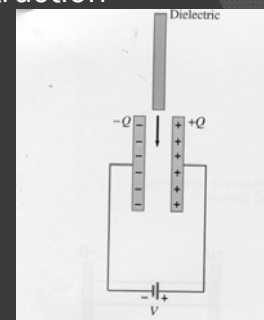
### Capacitor Construction

- Large capacitances achieved by:
  - large plate areas
  - insulators with high K
  - small separation of plates.
- Dielectric strength limits the reduction in spacing between plates and defines quality of the material as an insulator
- Potential gradient will withstand being punctured by a spark discharge




## Capacitors in Circuits (parallel)

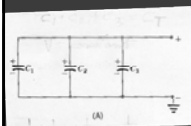


- $C_1, C_2, C_3$  in parallel
- 1 plate (of the capacitor) is attached to 1 conductor while another plate connected to a second conductor
- Same Voltage across all
- $q_1 = C_1 V$   $q_2 = C_2 V$   $q_3 = C_3 V$
- $q_T = q_1 + q_2 + q_3$
- $q_T = C_1 V + C_2 V + C_3 V$
- $q_T = C_T V$
- $C_T V = C_1 V + C_2 V + C_3 V$
- $C_T = C_1 + C_2 + C_3$
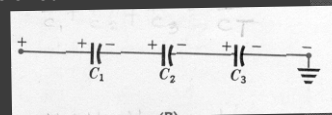
## Capacitors in Circuits (Series)

- $C_1, C_2, C_3$  in Series
- $q = q_1 = q_2 = q_3$
- Since charge is transferred
- $V_T = V_1 + V_2 + V_3$
- $V_T = q / C_T$
- $1 / C_T = 1 / C_1 + 1 / C_2 + 1 / C_3$




## Electric Current

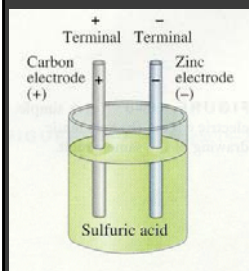

- Circa 1800
- Smackdown!!
  - Volta v Galvani
- We still refer to the type of battery he constructed as a Voltaic or Galvanic cell.
- It consists of 2 dissimilar metals as electrodes [carbon or platinum can serve as an "inert" electrode in place of one of the metals] immersed in an electrolyte [dilute solution of a strong acid or a nitrate solution of the metal serving as the electrode in that cell] and a connecting wire.
- The battery goes "dead" when chemical equilibrium is reached.

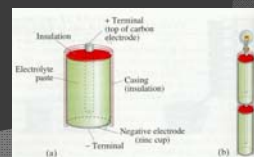
## Series and Parallel

- If you connect the + terminal of one battery to the - terminal of the next they are connected in **series**.
- If you link + to + and - to -, then they are in **parallel**


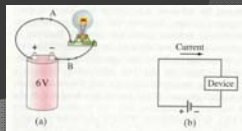
## Electric Current

- Electric Current—no longer static—electrons in motion!
- When we have a continuous conducting path between the terminals of a battery, we have an electric current.
- Note:
- the current flows from + to -.



## Electric Current

- **Electric current**—the net amount of charge that passes through it per unit time at any point.
- $I = \Delta Q / \Delta t$
- It's unit is the ampere, amp
- $A = 1 \text{ C/second}$
- In any single circuit, the current at any instant is the same at one point as at any other point since electric charge is conserved.