


Terminal Voltage, EMF, and Circuit Analysis

6 – ELETRIC CIRCUITS

EMF - \mathcal{E}

- A device
 - battery
 - electric generator
- that transforms one type of energy
 - chemical
 - mechanical
 - light
- into electrical energy is called a seat or source of electromotive force.
 - emf
 - \mathcal{E}



EMF

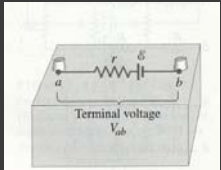
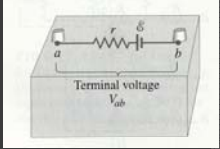



FIGURE 19-9 Diagram for an electric cell or battery.

- The potential difference between the terminals of such a source, when no current flows to an external circuit is called the emf of the source.
- It is not a force measured in Newtons—it's measured in VOLTS since it's a measure of potential difference.

EMF – Internal Resistance

- Every battery has **internal resistance** symbolized by r .
- If you turn on the headlights before you start the car, the lights dim. This is due to the internal resistance of the battery. (insufficient current flow)

Terminal Voltage

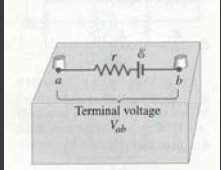


FIGURE 19-9 Diagram for an electric cell or battery.

- **Terminal voltage** –when there is no current drawn from the battery, $V_{ab} = \mathcal{E}$.
- Once you start to draw a current, I , the internal resistance of the battery kicks in.
- The actual voltage delivered is what we call the terminal voltage and is calculated:
- $V_{ab} = \mathcal{E} - Ir$

Kirchhoff's Rules

- Invented Mid-1800's to deal with complicated circuits.
- Based on the laws of conservation of charge and energy.

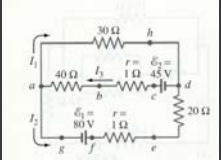


FIGURE 19-11 Currents can be calculated using Kirchhoff's rules.

Kirchhoff's First Rule


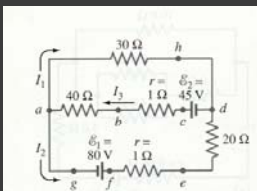


FIGURE 19-11 Currents can be calculated using Kirchhoff's rules.

- Junction Rule - At any junction point, the sum of all currents entering the junction must equal the sum of all currents leaving the junction.
- What goes in must come out!
- Conservation of Charge
- $I_1 + I_2 = I_3$


Kirchhoff's Second Rule

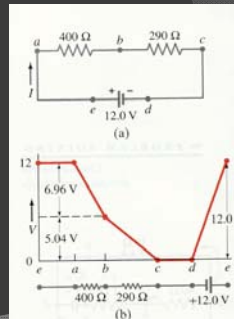- Loop Rule - The sum of the changes in potential around any closed path of a circuit must be zero.



- Conservation of Energy


Kirchhoff's Second Rule

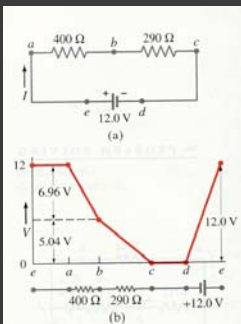

- $V = IR$
- $I = V/R = 12.0V/690\Omega$
- = .0174 A
- point e to point a no Δ
- a to b
 - $V=IR=400\Omega \cdot .0174A = -6.96V$
- b to c
 - $V=IR=290\Omega \cdot .0174A = -5.04V$
- c to d no Δ
- d to e $V = +12.0V$
- $12.0V - 6.96V - 5.04V = 0$

EMF in Series

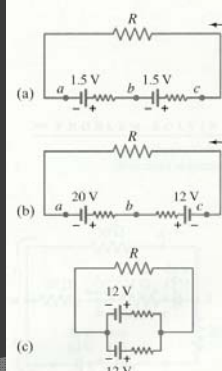- $\Sigma V = I \Sigma R$ in Series, resistances and Voltages add.
- a) $1.5V + 1.5V = 3.0V$
- b) One is backward!
 - Pick a direction
 - Follow the loop
 - Start at a, counter-clockwise
 - - to +, add (a to b, +20V)
 - + to -, subtract (b to c, -12V)
 - $+20 - 12 = 8V$
- If you wind up with a negative EMF, then the current is in the opposite direction.



EMF in Series

- b) Why Why Why?
- It seems silly to have an EMF in backwards,
- BUT this is how battery chargers and the alternators in cars work.
- It forces electrons to the negative terminal removing them from the positive.

